

ELECTRONICS WORLD



JULY 2006 £4.50

THE ESSENTIAL ELECTRONIC ENGINEERING MAGAZINE

POWER EVOLUTION
POE DESIGN
RESONANT NETWORKS
RLC SECTIONS



SONY'S CHALLENGES

THE TOUGH BALANCING ACT OF BEING ON TOP



**CORPORATE
PROFILE**
NEVER TOO
FAR FROM
TROUBLE



**TECHNOLOGY
NEWS**
SATELLITES WILL
OFFER BROADBAND
SERVICES



**WIRELESS
DATA**
6-IN-1
ANTENNA
FOR TRAINS

ALSO IN THIS ISSUE: DDS SIGNAL GENERATOR • INSIGHT • TOP TEN TIPS ON DSPS

Power Divider Rule


Generally, the Electrical Engineering studies have current and voltage divider formulae for circuit analysis and, also, some general formulae for power. But there is no specific formula for power such as current divider or voltage divider rule. This thought helped me to come up with the 'Power Divider Rule', which stipulates that: "The total dissipated power is equal to the total supplied power regardless of circuit configuration."

On the other hand, Norton and Thevenin had their own

way to measure the amount of current flow through any resistor. Although their way is different, their intention is the same. Hence, I came up with my way of finding the amount of power in any circuits.

It should be noted that the total power used by either circuit is the sum of its individual resistors' powers. Therefore, it is clearly proved that: "The total dissipated power is equal to the total supplied power regardless of circuit configuration."

Nachimani Charde
Malaysia

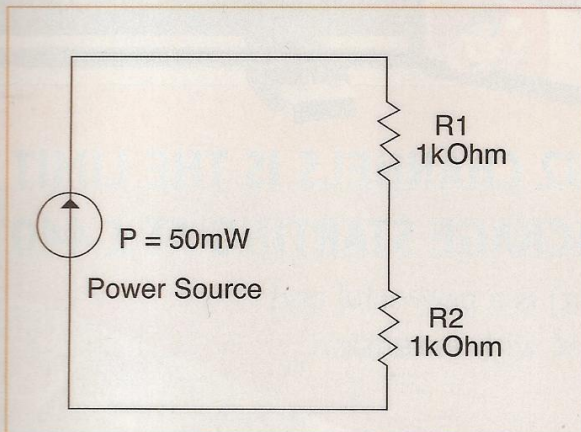

Series circuit analysis:


- 1) Power across Resistor 1

$$P_{R1} = \frac{P \cdot R1}{R1 + R2} = \frac{50m \cdot 1k}{1k + 1k} = 25mW$$

- 2) Power across Resistor 2

$$P_{R2} = \frac{P \cdot R2}{R1 + R2} = \frac{50m \cdot 1k}{1k + 1k} = 25mW$$

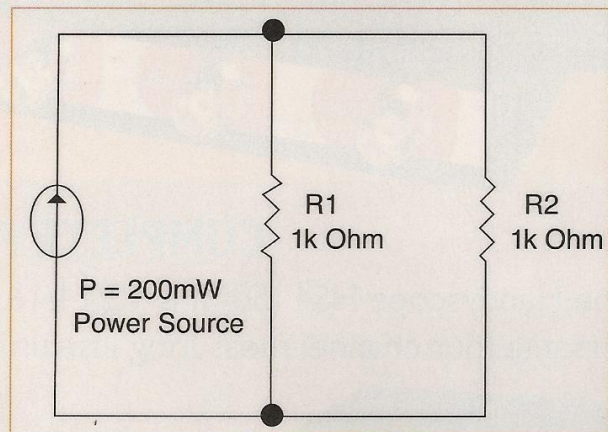- 3) Total Power: $P = P_{R1} + P_{R2}$
 $= 25mW + 25mW$
 $= 50mW$



Parallel circuit analysis:

- 1) Power across Resistor 1



$$P_{R1} = \frac{P \cdot R1}{R1 + R2} = \frac{200m \cdot 1k}{1k + 1k} = 100mW$$

- 2) Power across Resistor 2

$$P_{R2} = \frac{P \cdot R2}{R1 + R2} = \frac{200m \cdot 1k}{1k + 1k} = 100mW$$

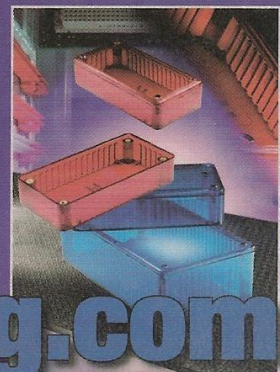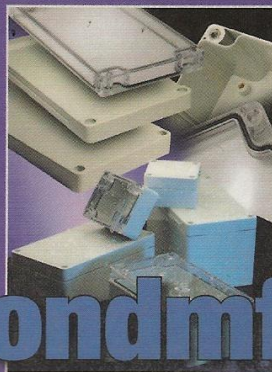- 3) Total Power: $P = P_{R1} + P_{R2}$
 $= 100mW + 100mW$
 $= 200mW$

HAMMOND
MANUFACTURINGTM
Die-cast aluminium,
metal and plastic
enclosures
+ 44 (0)1256 812812
sales@hammond-
electronics.co.uk



www.hammondmfg.com